



THE UNIVERSITY
of ADELAIDE



CRICOS PROVIDER 00123M


School of Computer Science

COMP SCI 2000 Computer Systems Lecture 3

adelaide.edu.au

seek LIGHT

The whole system

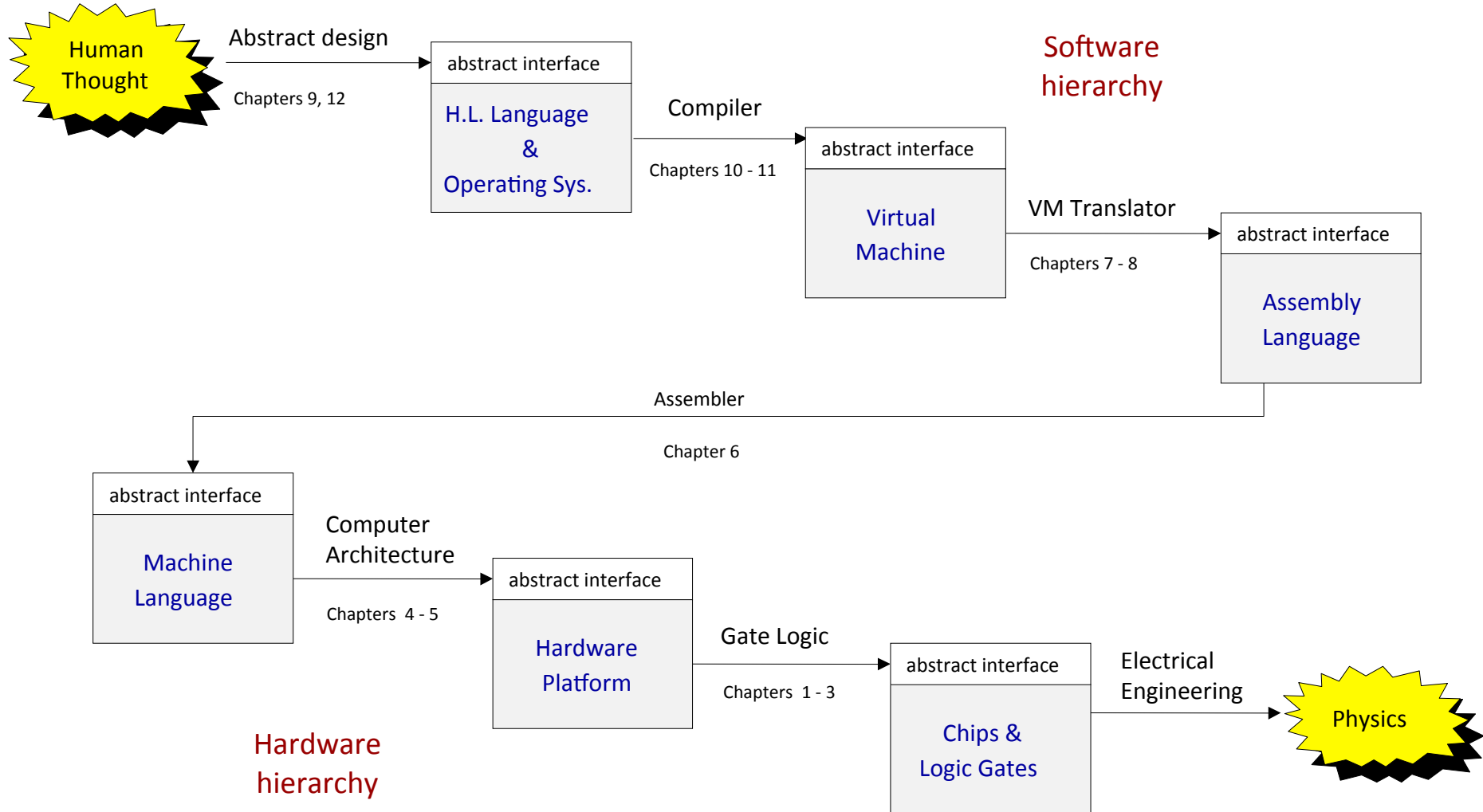


(Abstraction–implementation paradigm)

Review: What is gate logic?

- Our hardware is an inter-connected set of chips.
- Chips are built of simpler chips, down to the simplest structure of all – the elementary logic gate.
- Logic gates are hardware implementations of Boolean functions. This allows us to represent logical statements in computer form.
- Every chip and gate has:
 - An interface: Telling us what it does
 - An implementation: Telling us how it does it.
- Worksheet Question 1:
 - In 1-2 sentences write why interfaces are important.


Review: Example

Interface

 

a	b	out
0	0	0
0	1	1
1	0	1
1	1	0

Implementation

 

All Boolean functions of 2 variables

Function	x	0	0	1	1
	y	0	1	0	1
Constant 0	0	0	0	0	0
And	$x \cdot y$	0	0	0	1
x And Not y	$x \cdot \bar{y}$	0	0	1	0
x	x	0	0	1	1
Not x And y	$\bar{x} \cdot y$	0	1	0	0
y	y	0	1	0	1
Xor	$x \cdot \bar{y} + \bar{x} \cdot y$	0	1	1	0
Or	$x + y$	0	1	1	1
Nor	$\overline{x + y}$	1	0	0	0
Equivalence	$x \cdot y + \bar{x} \cdot \bar{y}$	1	0	0	1
Not y	\bar{y}	1	0	1	0
If y then x	$x + \bar{y}$	1	0	1	1
Not x	\bar{x}	1	1	0	0
If x then y	$\bar{x} + y$	1	1	0	1
Nand	$\overline{x \cdot y}$	1	1	1	0
Constant 1	1	1	1	1	1

Do Lecture 3
worksheet
question 2.

What can we build from NAND?

- What is NAND?



What can we build from NAND?

- What is NAND?
 - NOT AND(a,b)
- Think about how could we build:
 - NOT from NAND?
 - TRUE if we have NAND and FALSE?
 - AND from NAND?
 - OR from NAND?
 - XOR from NAND?

Review: Gate logic


- Gate logic – a gate architecture designed to implement a Boolean function

- Elementary gates:

  


- Composite gates:

Gate interface

 


Gate implementation

 

- Important distinction: Interface (*what*) VS implementation (*how*).
-

Project 1: Multiplexer

a	b	sel	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

 

sel	out
0	a
1	b

Proposed Implementation: based on Not, And, Or gates.

What does this *do*? What is a multiplexer?

Example: Building an **And** gate



And.cmp

a	b	out
0	0	0
0	1	0
1	0	0
1	1	1

Contract:

When running your **.hdl** on our **.tst**, your **.out** should be the same as our **.cmp**.

And.hdl

```
CHIP And
{
  IN  a, b;
  OUT out;
  // implementation missing
}
```

And.tst


```
load And.hdl,
output-file And.out,
compare-to And.cmp,
output-list a b out;
set a 0, set b 0, eval, output;
set a 0, set b 1, eval, output;
set a 1, set b 0, eval, output;
set a 1, set b 1, eval, output;
```

What can we build from NAND?

- What is NAND?
 - NOT AND(a,b)
- How could we build:
 - NOT from NAND?
 - TRUE if we have NAND and FALSE?
 - AND from NAND? (Spoiler Alert!!!!)
 - OR from NAND?
 - XOR from NAND?

Building an **And** gate

 Implementation: $\text{And}(a,b) = \text{Not}(\text{Nand}(a,b))$




And.hdl

```
CHIP And
{
  IN  a, b;
  OUT out;
  // What goes in here?
}
```

Building an **And** gate

 Implementation: $\text{And}(a,b) = \text{Not}(\text{Nand}(a,b))$



And.hdl

```
CHIP And
{
  IN  a, b;
  OUT out;


  Nand(a = a,
        b = b,
        out = x);
  Not(in = x, out = out)
}
```

Hardware Simulator – Demo!

Try worksheet
question 3

Quick stop!

 - Each Boolean function has a canonical representation
- The canonical representation is expressed in terms of And, Not, Or
- And, Not, Or can be expressed in terms of Nand alone
- Every Boolean function can be realized by a standard circuit consisting of Nand gates only
- Mass production
- Universal building blocks, unique topology
- Gates, neurons, atoms, ...



Counting systems

quantity	decimal	binary	3-bit register
	0	0	000
*	1	1	001
**	2	10	010
***	3	11	011
****	4	100	100
*****	5	101	101
*****	6	110	110
*****	7	111	111
*****	8	1000	overflow
*****	9	1001	overflow
*****	10	1010	overflow

Answer
worksheet
question 4

Binary Addition

Assuming a 4-bit system:

$$\begin{array}{r} \textcolor{red}{0} \text{ } \textcolor{red}{0} \text{ } \textcolor{red}{0} \text{ } \textcolor{red}{1} \\ \hline 1 \text{ } 0 \text{ } 0 \text{ } 1 \\ 0 \text{ } 1 \text{ } 0 \text{ } 1 \\ \hline \textcolor{red}{0} \text{ } 1 \text{ } 1 \text{ } 1 \text{ } 0 \end{array} \quad +$$

no overflow

$$\begin{array}{r} \textcolor{red}{1} \text{ } \textcolor{red}{1} \text{ } \textcolor{red}{1} \text{ } \textcolor{red}{1} \\ \hline 1 \text{ } 0 \text{ } 1 \text{ } 1 \\ 0 \text{ } 1 \text{ } 1 \text{ } 1 \\ \hline \textcolor{red}{1} \text{ } 0 \text{ } 0 \text{ } 1 \text{ } 0 \end{array} \quad +$$

overflow

- Algorithm: exactly the same as in decimal addition
 - Overflow (MSB carry) has to be dealt with.
 - How do we represent negative numbers? (Group work worksheet question 5)
-


Building an Adder chip



- Adder: a chip designed to add two integers
 - Proposed implementation:
 - Half adder: designed to add 2 bits
 - Full adder: designed to add 3 bits
 - Adder: designed to add two n -bit numbers.
-

Half adder (designed to add 2 bits)


a	b	sum	carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

Implementation: based on two gates that you've seen before.
What do you think they are? (Group discussion: Worksheet question 6)

Full adder (designed to add 3 bits)

a	b	c	sum	carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

Implementation: can be based on half-adder gates. How?
(exercise for after the lecture).

Perspective

- Combinational logic
 - Our adder design is very basic: no parallelism
 - It pays to optimize adders (but we won't do that here).
 - Where is the seat of more advanced math operations?
a typical hardware/software tradeoff.
-

Summary

- You can construct many gates from NAND – this is just one example of how gates are built up.
- By understanding arithmetic, we can combine gates to add two numbers, then combine half-adders to add larger numbers.

Next week

- There is a lecture on Monday!
- There is a tutorial next week.
- Make sure you get familiar with the hardware simulator!
- You should read “Chapter 3” from the forums and keep working on your Assignment 1.
 - Remember there is a milestone due!
- Any questions? Ask on the forum or right now!